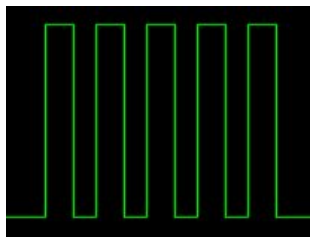


[Home](#) | [Products](#) | [Custom Electronics](#) | [Science](#) | [Contact Us](#)
[Home](#) ▸ [Projects](#) ▸ [DIY Devices](#) ▸ [DIY Signal Generator](#)
[Home](#)[Contact Us](#)[Shop](#)[Projects](#)[DIY Devices](#)[DIY Plasma Globe](#)[DIY Mini Tesla Coil](#)[DIY Kirlian Photos](#)[DIY SRSG Tesla Coil](#)[DIY Plasma Gun](#)[DIY Power Pulse Generator](#)[DIY Ignition Coil Driver](#)[DIY Voltage Multiplier](#)[DIY Power Pulse Controller](#)[DIY Van De Graff Generator](#)[DIY PWM Signal Generator](#)[DIY Signal Generator](#)[DIY Puppet Animator](#)[DIY Robot \(MIRC\)](#)[DIY Sensor Multiplexer](#)[DIY Tesla Coil Tuner](#)[DIY HHO Hydrogen Production](#)[DIY Jet Engine](#)[DIY Electrohydrodynamic Thruster](#)[DIY Magnetohydrodynamic Thruster](#)[DIY Outboard Motor](#)[DIY Cymatics Display](#)[DIY Super Cooler](#)[DIY Dehumidifier](#)[DIY Underwater Camera](#)[DIY Vacuum Chamber](#)[DIY Plasma Gun II](#)[DIY Induction Heater](#)[DIY Robot II](#)[DIY High Speed Flash](#)[Simple Science Experiments](#)[Science](#)[Research](#)[Custom Electronics](#)

A Tiny Homemade Square Wave Signal Generator ('Dead Bug' Style)





This page shows you how to make a super simple square wave signal generator. The circuit below uses a 555 timer chip, a capacitor, and some resistors to generate a variable frequency, variable pulse width square wave. The term 'dead bug' refers to the way that the finished circuit resembles a dead insect. This is because the solder connections are made directly to the components and there are legs sticking out making it look much more messy than the diagram below.

This is a very basic circuit and therefore does not produce an ideal square wave over the full frequency range. The pulse width or duty cycle can only be varied by a small amount, and doing so also

affects the frequency output.

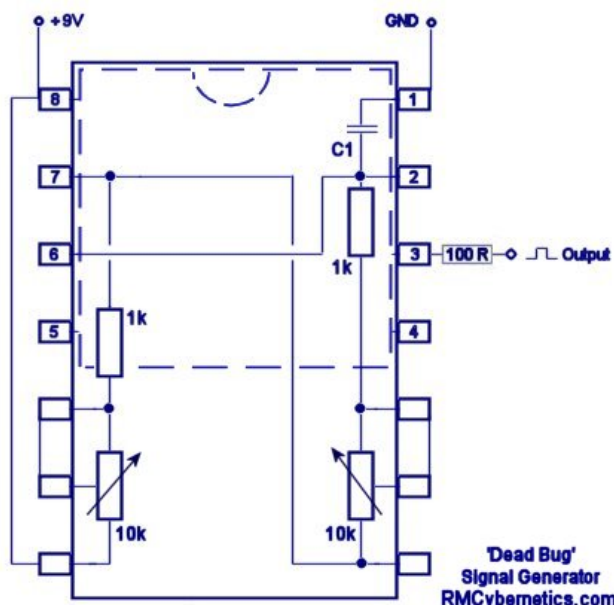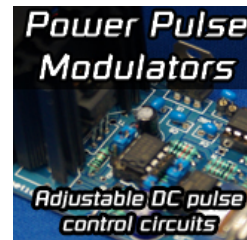If you want to try a more advanced and more accurate version see the [DIY Signal Generator II](#)



This diagram shows how the circuit can be wired without the need for any circuit board. A 14 pin IC socket is used to hold the main circuit so the 555 chip and the two pots can be simply plugged in. The total parts list is shown below.

14 pin IC Socket
NE555N Timer IC
1k Resistors x2
10k Variable Resistor/ Potentiometer x2
[Capacitor selection for C1](#)

If you want to switch loads like coils, motors and lights, our range of [Cyber Circuits](#) are for you!

The diagram represents a view from below and is not to scale. The circuit may be a little tricky to solder, but its about as simple as you can get for a signal generator.

This circuit can be used in the [DIY Tesla Coil](#) project as part of the [Ignition Coil Driver](#)

The value of the capacitor C1 will determine the range of frequencies produced. Somewhere around 0.1 to 0.01 microfarads should be adequate for mid range audio frequencies.





Check our facebook page for updates and special offers

165

facebook

Like

Send

Comments and questions for DIY Signal Generator

The information provided here can not be guaranteed as accurate or correct. Always check with an alternate source before following any suggestions made here.

james - Saturday, 30th December 2006 10:13am - #647

would this circuit be suitable for a auto transformer or car coil?

RMCybernetics - Saturday, 30th December 2006 4:23pm - #648

It would provide an adequate signal, but a large transistor would be needed for switching the power. You can see examples on the [ignition coil driver](#) page or the [power pulse controller](#) page.

geneotype - Sunday, 16th September 2007 3:58pm - #1718

dear rmc i have made quite a few square wave circuits in my time but no have worked. my power supply is that of a car battery charger 12v . i have noticed that it oscilates a little as most chargers do. would this affect my square wave circuits indering their performance? please reply soon as im hanging off the end of my chair to know thank you, sincerely geneotype.

RMCybernetics - Sunday, 16th September 2007 7:10pm - #1721

Yes it would. You need to use a proper DC supply or a battery.

geneotype - Wednesday, 19th September 2007 1:08am - #1737

ohh thank goodness i thought that i was so bad at electronics that every time i tryed the same circuit it never worked now i know why thank you now i wish i had of tryed dc inseed of building the same circuit over 26 times spending 0 for a \$ 4 circuit thankyou

genotype - Tuesday, 25th September 2007 11:41am - #1751

dear rmc is there a transistor other than the 2n3055 that would work in the self resonation circuit for a flyback? high speed switching and heavy current loadig.

RMCybernetics - Tuesday, 25th September 2007 11:59am - #1752

A similar rated one might be TIP142 100V 10A. A MOSFET type IRF740 400V 10A would also work

Ben - Wednesday, 31st October 2007 10:33am - #2093

RMC, fantastic pages here and a huge amount of patience for people on a steep learning curve like me!
Could C1 be changed to a value that would allow an IRF740 to switch a LED for testing. i.e. so you can see it flicker?
Also, feel really stupid here, which way round do I mount C1 and how do I tell the + side of the cap?

Many thanks
ben

RMCybernetics - Wednesday, 31st October 2007 1:59pm - #2095

Most caps are non polarized (there is no specific + or -). One which have larger capacity tend to be polarized and the pins are clearly marked. Typically these are electrolytic or tantalum capacitors. The -ve leg of such a capacitor would connect to GND in this circuit. Capacitors larger than 100nF will allow you to see the output if connected to an LED.

Ben - Wednesday, 31st October 2007 9:00pm - #2100

It worked well and flashed at approx 2hz. Without a cap, i just upped the resitance/s which I figured from a handy 555 timer program. Thing is, when I connected it to my coil the 555 gave up. I had connected a cap and resistor as a snubber across the coil. also a zener 5W 15volt from the irf740 mosfet to ground. Do you know what went wrong?

Thanks again
Ben

RMCybernetics - Thursday, 1st November 2007 12:15pm - #2104

This circuit will not drive any coils by its self. It only provides signal. Maybe you should look at the [ignition coil driver](#).

dave - Wednesday, 28th November 2007 10:26pm - #2257

Could you help me with a few queries on the 'Dead bug' signal generator;

> What is the 100R next to the output of this circuit?

> Does a 1k resistor refer to a 1000 ohm resistor (1 k ohm)?

> Can any potentiometer be used as a variable resistor, or are they different components?

> Does the 9v input come from the positive battery terminal? If so, where is the negative battery terminal connected to?

many thanks.

RMCybernetics - Thursday, 29th November 2007 11:18am - #2264

The 100R refers to a 100 ohm resistor used to limit the current flowing from the signal output.

Yes 1k is 1000 ohms resistor.

Any potentiometer with the same resistance value will work. The one used here is a linear type.

Yes 9V is +ve battery terminal. -ve terminal goes to GND

dave - Friday, 30th November 2007 9:19am - #2277

What Wattage resistor (I wasn't aware resistors had watts. the ones i've found are either 2, 7, 10 watts) would be suitable for the 1k resistors of the 'dead bug' signal generator, the 100 ohm resistor of the 'dead bug', the 10k resistor of the driver circuit, and the 100 ohm resistor of the driver circuit?

And once the 'dead bug' circuit is complete, how do the potentiometers operate? (what do they do, or what should I do to them).

cheers.

RMCybernetics - Friday, 30th November 2007 9:35am - #2278

This value just refers to the amount of power it can handle. The power in this circuit is tiny so it does not matter what value you use.

newbie - Friday, 18th January 2008 3:58am - #2451

how do you connect the potentiometer?

RMCybernetics - Friday, 18th January 2008 2:26pm - #2458

If you have vertical mount miniature presets, you can just plug them into the IC socket. If not, you will need to add leads to the pins and insert them into the socket.

Ryan - Monday, 28th July 2008 3:57pm - #2950

What if you want a sine wave with a constant amplitude over a varying frequency range like a sweep tone generator

Frank - Tuesday, 19th August 2008 4:21am - #3004

I have tried many different circuits similar to this, I've success and the circuits have failed miserably. In this circuit, pin 4 is disconnected to the positive rail. Why?

RMCybernetics - Tuesday, 19th August 2008 1:37pm - #3007

Because of laziness I suppose :) Most versions of a 555 will work when the reset pin is left unconnected, but it is probably better if you connect it to V+

imbecile - Sunday, 16th November 2008 7:48pm - #3353

can this circuit be used as an RF transmitter, i mean to use it to drive a single switching transistor?

RMCybernetics - Sunday, 16th November 2008 8:11pm - #3355

Yes

Paul - Thursday, 12th February 2009 3:43pm - #3566

Hi RMC there is a diagram for a sine wave gen. I want to make a low wattage induction heater the coil uses high frequency AC voltage can this be simulated with a sine gen and a power amp on an ignition coil to drive the induction coil. thanks Paul

RMCybernetics - Friday, 13th February 2009 2:04pm - #3570

Induction heaters are driven with a square wave driver. The resonant inductor-capacitor circuit oscillates in a sine wave when the square wave input is the right frequency.

Continuum - Saturday, 28th February 2009 5:19pm - #3603

Hey RMC, I was wondering. When using a 9V battery how do I establish a ground? Is it simply using the -9V end as ground?

Steve ford - Monday, 2nd March 2009 8:36pm - #3604

Can this circuit be used to drive an injector driver such as a LM1949? I will need to be running 5 x LM1949's powering 5 injectors simultaneously. Also can this circuit be powered off 12V? if so what will the output voltage be?

Thanks

Steve

RMCybernetics - Tuesday, 3rd March 2009 10:15am - #3613

Continuum,

There is no -9V connection really. Voltages are relative. If you say the negative terminal is -9V then the positive one would be 0V.

Typically the negative connection is used as 0V or ground while the positive is +9V.

Steve ford,

It can but you will need to use resistors to make a voltage divider on the 555's output so it will match the LM1949's input requirements.

The 555 will work from 12V, but then the output would also be 0 to a bit less than 12V.

Brian - Friday, 6th March 2009 2:36am - #3628

Hi RMC,

Could you label the NE555N pin connections? According to my STMicroelectronics NE555N chip data sheet, the circuit wiring above is mirrored what it should be (it connects +9V to the gnd pin, gnd to the Vcc pin and so on.. see image). I didn't catch this in time and burnt my chip out. Just don't want this to happen to someone else.

Thanks!

RMCybernetics - Friday, 6th March 2009 6:29am - #3631

Mirrored? Look at the pin numbers and also where it says "The diagram represents a view from below"

Brian - Friday, 6th March 2009 2:31pm - #3632

Also, do we need anything to limit the current going into the chip? I don't get why the chip burnt out so quickly.

Greg - Saturday, 7th March 2009 1:22am - #3634

Do you need to use a NE555N timer or can you use other timers of the NE555 family? I could only find a NE555P at my local RadioShack but it doesn't seem to be working.

RMCybernetics - Saturday, 7th March 2009 9:24am - #3635

If the pinout and voltage spec is the same, you can use it

RMCybernetics - Wednesday, 22nd April 2009 1:21pm - #3775

Brian,
No, the 100 ohm resistor on the output is used for limiting current. If you are driving a low impedance load, maybe you should increase the resistance of this.

Petech - Wednesday, 30th September 2009 10:14pm - #4064

Can i use this circuit as a receiver circuit for rf remote control? and what should i alter to achieve this

RMCybernetics - Sunday, 11th October 2009 10:59am - #4071

No. You need a totally different circuit.

Harengus - Monday, 18th January 2010 6:19pm - #4189

Can this circuit be used to control a pair of lcd shutter glasses? I need them to "open" for periods of about 10ms at about 4Hz.

RMCybernetics - Monday, 18th January 2010 8:31pm - #4191

Yes. You would need to calculate the resistor capacitor combination for your specific timing needs.

Electronics Novice - Thursday, 6th May 2010 12:36pm - #4366

I need to generate a 24v dc signal at a frequency of 27hz. What is the output signal/voltage of this circuit and can I use this to operate a relay???

RMCybernetics - Monday, 10th May 2010 9:49pm - #4369

This can only operate up to about 15V. For 24V operation you should use a 12V regulator to supply the circuit. For switching a relay you will also need a small transistor to amplify the current for the relay coil.

Electronics Baby - Tuesday, 11th May 2010 2:26am - #4370

Hi. Great site, thank you :)

I would like to add a 2N3055 to this circuit to pulse a coil.

1. Is this possible ?
2. What would go from the 555 to the 3055, just the output pin-3 ?

Thank you :)

noob - Wednesday, 12th May 2010 3:42pm - #4372

Hi.

If someone could put a picture of this circuit on a breadboard i would be really grateful.

Thanks if you can :)

Vilemeister - Tuesday, 14th December 2010 4:19pm - #4460

This seems to have died, however i'll post my experiences. I just built this circuit with a 555 timer signal supply with 1 ignition coil. It works very well, however the 555 keeps burning out after 10 seconds or so of running. I need to get CMOS timers and put series resistors in. noob, I can take a picture of my breadboard and send it to you if you want.

RMCybernetics - Sunday, 19th December 2010 8:55pm - #4463

555 timers usually pop from voltage spikes in ignition coil circuits. You need to add a voltage regulator or TVS to protect it

Arex - Saturday, 2nd April 2011 3:51am - #4534

You deserve a medal for extreme patience , RMC.

RMCybernetics - Saturday, 2nd April 2011 6:02am - #4535

Hehe, thanks! Over 4500 messages now :D

Raj - Monday, 21st November 2011 7:46am - #4674

help.. 555 timers usually pop with in 2seconds..when 12v 7amps power is supplied even after adding a voltage regulator..plz help me what is the reason for it n what should i do to stop pop of NE555 Thanks

Add Your Comment

Click the button to leave your comment or question

© Copyright RMCybernetics